BCS GOVT PG COLLEGE DHAMTARI

Assignment - 2019-20

B.Sc. - II Year

Information Technology

(Digital Circuits and Computer Hardware)

PAPER-I

Date - 07-10-2020	Max Marks-50
All questions carry equal marks.	
1. WHAT IS K-Map? EXPLAIN WITH EXAMPLE?	
2. What is Flip-Flop? Explain different types of Flip-Flop?	
3. What is Integrated Circuits? Explain RTL and TTL Integrated Circ	cuits?
4. Explain all types of Addressing Modes with suitable example?	
5. What is difference Between Cache memory and Virtual memor	·y?