

Roll No. ....

**E-304**

**M. Sc. (First Semester)  
EXAMINATION, Dec.-Jan., 2020-21**

**PHYSICS  
Paper Fourth  
(Electronics)**

*Time : Three Hours ]*

*[ Maximum Marks : 80*

**Note :** Attempt all Sections as directed.

**Section—A**

1 each

**(Objective/Multiple Choice Questions)**


**Note :** Attempt all questions.

Choose the correct answer :

1. Which one is not a characteristic of an ideal OPAMP ?
  - (a) Bandwidth frequency is infinite
  - (b) Voltage gain is zero
  - (c) Input impedance is infinite
  - (d) Output impedance is zero
2. At the Virtual Ground Point (VGP) of OPAMP :
  - (a) Only potential difference between VGP and ground is nil

**P. T. O.**

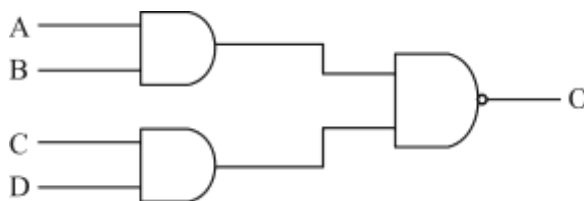- (b) Only impedance between VGP and ground is nil
- (c) Both (a) and (b)
- (d) None of these
3. One of the applications of OPAMP as a linear device is in :
- (a) Comparator
- (b) Waveform generator
- (c) Schmidt trigger
- (d) Integrator
4. Common mode rejection ratio of a good OPAMP is :
- (a) Less than 1
- (b) Equal to 1
- (c) Very large
- (d) Equal to the common mode gain
5. What is the output of circuit shown in figure below ?



O =

- (a)  $\overline{A B C D}$
- (b)  $\overline{A B + C D}$
- (c)  $(\overline{A} + \overline{B})(\overline{C} + \overline{D})$
- (d) None of these

6. The simplified form of logic expression :

$$\overline{A}B + AB + \overline{\overline{A}B} + AB$$

- (a) A
  - (b) B
  - (c) AB
  - (d) 1
7. The ..... gate is used as a two-bit comparator.
- (a) AND
  - (b) OR
  - (c) NAND
  - (d) EX-OR
8. The NAND and NOR gate are called the :
- (a) Universal gates
  - (b) Basic gates
  - (c) Hexadecimal gates
  - (d) Decimal number gates
9. A sequential circuit consists of :
- (a) Combinational logic only
  - (b) Memory element only
  - (c) Both (a) and (b)
  - (d) None of these
10. Flip flops are :
- (a) Monostable elements
  - (b) Bistable elements
  - (c) Astable elements
  - (d) Tristable elements

11. Main building blocks of memory are :
- (a) Multiplexers
  - (b) Decoders
  - (c) Encoders
  - (d) Registers
12. In a clocked SR flip flop, R is connected with S through an inverter, the circuit is also called :
- (a) JK flip flop
  - (b) D flip flop
  - (c) T flip flop
  - (d) None of these
13. Which of the interrupts of  $\mu$ p 8085 has the highest priority ?
- (a) TRAP
  - (b) INTR
  - (c) RST 7.5
  - (d) RST 6.5
14. How many flags are available with  $\mu$ p 8085 ?
- (a) 6
  - (b) 5
  - (c) 4
  - (d) 3
15. The rotate operations are performed in ..... register.
- (a) Accumulator
  - (b) B Register
  - (c) SP registers
  - (d) PC registers

16. Which of the following instructions is used to save the content of the accumulator in the stack ?
- (a) PUSH PSW
  - (b) PUSH A
  - (c) POP A
  - (d) POP PSW
17. Which one of the given instructions is one-byte instruction ?
- (a) MVI A, 85H;
  - (b) LHLD 2500H;
  - (c) STAX B;
  - (d) IN 29H;
18. If the  $\mu$ p 8085 adds two byte data : 87H and 79H—which flag(s) will be set (i.e. become(s) 1) :
- (a) Zero flag
  - (b) Aux. carry flag
  - (c) Carry flag
  - (d) All of these
19. Which instruction sequence is equivalent to the XCHG instruction ?
- (a) PUSH H and POP D
  - (b) PUSH D and POP H
  - (c) PUSH H; PUSH D; POP H; POP D
  - (d) None of these

20. The stack in memory is defined by initializing the ..... register.
- (a) Program Counter (PC)
  - (b) Stack Pointer (SP)
  - (c) Both PC and SP
  - (d) None of PC and SP

**Section—B**

2 each

**(Very Short Answer Type Questions)**

**Note :** Attempt all questions.

1. What is an OP-AMP ? Why is it called so ?
2. Define the term Common Mode Rejection Ratio (CMRR) of an OPAMP.
3. Write the truth table of EXNOR gate.
4. What is race around condition in the JK flip flop ?
5. What do understand by Edge triggered flip flop ?
6. What is the function of program counter in the  $\mu\text{p}$  8085 ?
7. What is a stack memory ? On what principle does it work ?
8. What is a counter ? How many flip flops are required to construct a decade counter ?

**Section—C**

3 each

**(Short Answer Type Questions)**

**Note :** Attempt all questions.

1. Convert a hexadecimal number  $(8000)_{16}$  into a decimal number.

2. Determine the output voltage of an OPAMP for  $v_1 = 150 \mu\text{V}$ ,  $v_2 = 140 \mu\text{V}$ . Differential gain  $A = 4000$  and Common Mode Rejection Ratio (CMRR)  $P = 100$ .
3. Simplify the Boolean function :

$$Z = \overline{A} \overline{B} C + \overline{A} B \overline{C} + \overline{A} B C + A \overline{B} C + A B C$$

4. Realize a JK flip flop using SR flip flop and write its state equation.
5. Write four/five steps of PUSH operation which pushes contents of B and C registers into stack.
6. List down the types instructions of  $\mu\text{p} 8085$  and explain each in one sentence.
7. Write down the content of register A, after executing the following program and explain :

MVI A, 55 H;

MVI B, 25 H;

ADD B

HLT

8. Compute as to how many times the loop in the following program is executed :

LXI D, 00 50H ;

LOOP : DCX D

MOV A, E ;

ORA D ;

XRA A ;

JNZ LOOP ;

HLT

## Section—D

5 each

## (Long Answer Type Questions)

**Note :** Attempt all questions.

1. Derive the expression for close-loop gain of an OPAMP in non-inverting voltage feedback configuration.

*Or*

Give the truth table of an EXOR gate and highlight its various applications.

2. What are the universal gates ? Why are they named so ? Derive the basic gates (*i.e.*, AND, OR and NOT gates) from any *one* of universal gates.

*Or*

Draw the ckt of MS JK flip flop and explain its function.

3. Draw the block diagram of  $\mu$ p 8085 and explain the functions of various registers in general and the accumulator in special.

*Or*

What are the various flags available in 8085 ? Describe their roles and significances.

4. Write an Assembly Level Program (ALP) of  $\mu$ p 8085 along with its flowchart to add two one byte numbers already stored in addresses F800H and F801H. Store the result in the locations F802H and F803H.

*Or*

Write and assembly level program of  $\mu$ p 8085 along with its flow chart to multiply two one byte numbers already stored in addresses F800H and F801H. Store the results in the locations F802 and F803H.